

# Project presentation

Marcel Konieczny

March 1, 2024

# Contents

- 1 Introduction
- 2 Board manufacturing
  - Schematic
  - LTSpice
  - PCB
- 3 Measurements
  - Problems
  - measurements
- 4 Conclusions

# Project assumptions

## Main project assumptions


- Microprocessor system
- Gas sensor TGS8100
- LCD Display

# Gas sensor TGS8100


## Sensor characteristics


- Low power consumption (heater power consumption 15mW)
- Long life
- Highly sensitivity to cigarette smoko, cooking odors and gaseous air contaminants
- Applications: air cleaners, air quality monitors, ventilation control

# How it works?


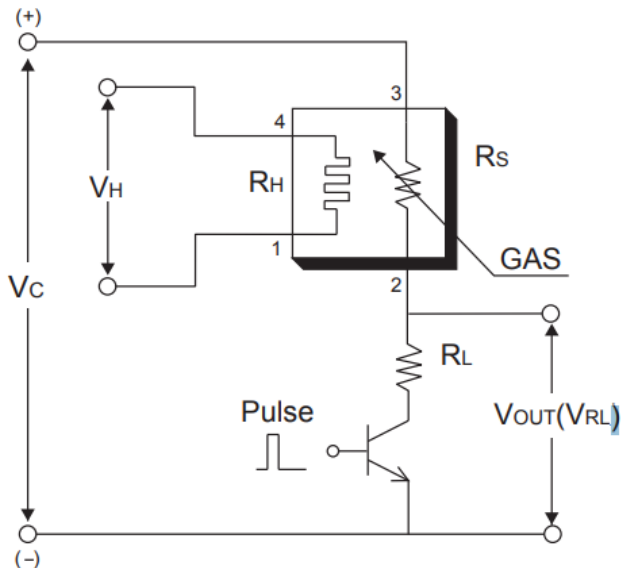


# Schematic

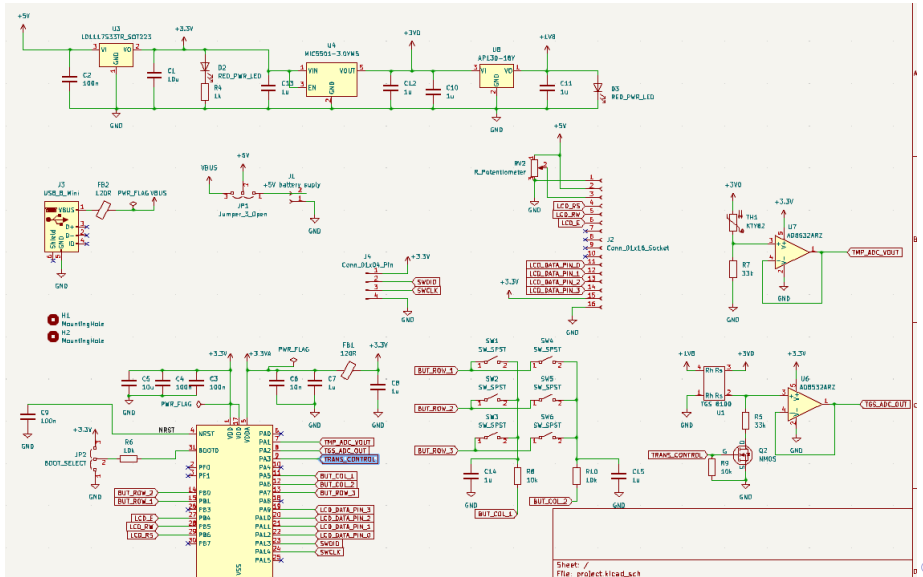

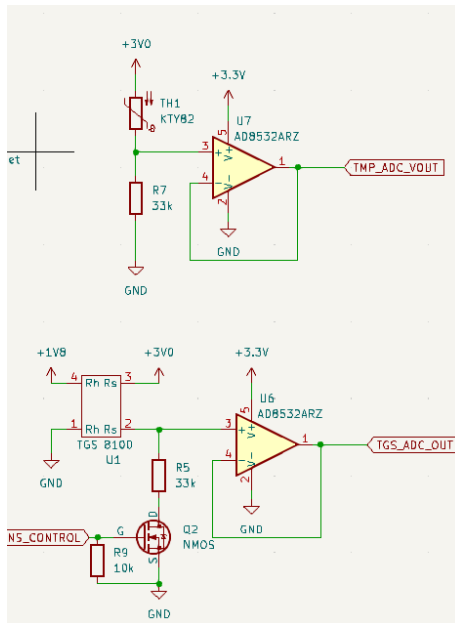


# LTSpice simulations

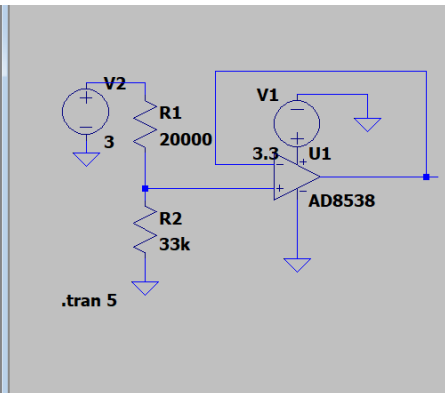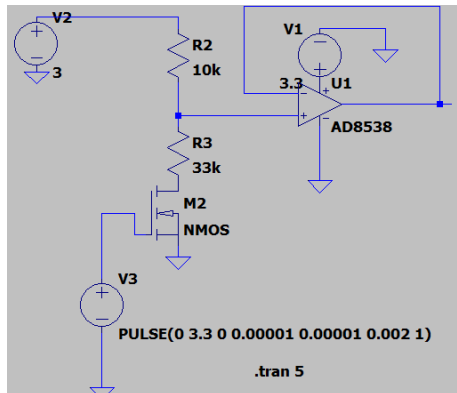




# TGS8100 simulations

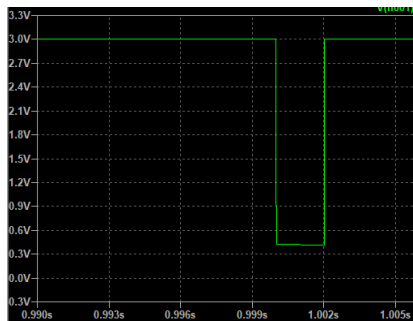

$R = 10\text{k}\Omega$

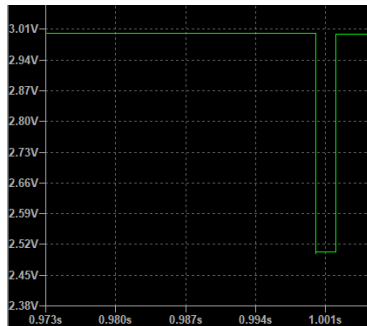

$R = 300\text{k}\Omega$

# Temperature sensor simulations




$R = 2k\Omega$  (25 °C)



$R = 1922\Omega$  (20 °C)

## PCB

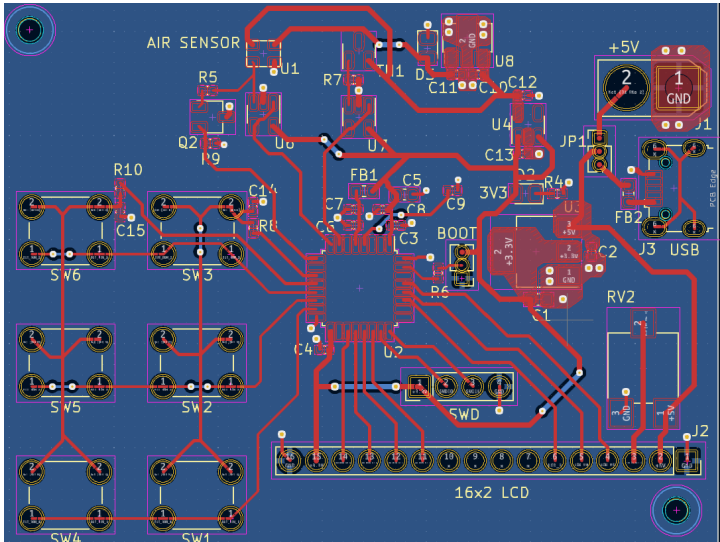

# Measurements

The following measurements are done:

- Internal VRef channel measurement to calculate ADC VRef
- Temperature measurements
- Voltage measurement (without tgs8100 sensor)

▼ temp_sensor	TEMP_SENSOR	{...}
(x)= adc_channel	uint16_t	1
(x)= raw_val	uint16_t	3143
(x)= updated	uint8_t	1 '\001'
(x)= temp	double	22.517666539559158

# Problems

During measurements the following problems were discovered

- Wrong footprints of elements
- Wrongly selected temperature sensor (measure range -55 to 150)

# Conclusions

- Temperature sensor is measuring quite correctly
- Pay attention to simulations
- Pay attention to properly choose footprints

Thank you for attention